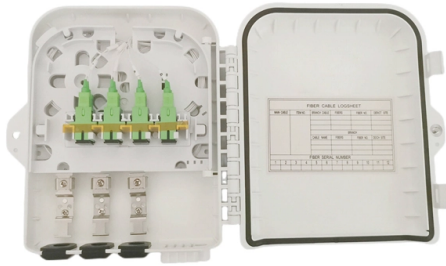


## Wiring of the 18-circuit distribution box



### Overview

Distribution Box and Selection Guide: Internal Structure, Components. Learn how to choose a distribution box and understand its internal structure, inclu.

### Key Takeaways

An 18-circuit distribution box is wired by connecting the incoming supply to the main switch, then distributing power through protective devices to each circuit, with neutrals and earths properly linked and all circuits clearly labeled. Components Overview

An 18-circuit distribution box typically includes:

- Main switch or double-pole MCB to control the incoming supply.
- RCCB or RCD for leakage and shock protection.
- MCBs or RCBOs for each of the 18 outgoing circuits.
- Neutral bar to distribute neutral connections.
- Earth bar for grounding all circuits.
- Busbars for phase distribution.



- Optional Surge Protective Device (SPD) if required by risk assessment .

#### Wiring Sequence

- Incoming Supply Connection: Connect the phase and neutral from the utility or meter to the main switch or isolator. This acts as the primary control for the entire board .
- RCCB/RCD Connection: The output of the main switch feeds the input of the RCCB. The RCCB protects against leakage currents and electric shocks .
- Branch Circuit Distribution: Connect the output of the RCCB to the input terminals of the 18 MCBs or RCBOs. Each MCB protects an individual circuit .
- Neutral and Earth Wiring: Connect all neutral wires from the loads to the neutral bar, and all earth wires to the earth bar. Ensure the supply neutral and earth are also linked to these bars .
- Wire Management: Route wires neatly, typically with branch wiring on the left and outgoing wiring on the right. Use plastic ties to keep wires straight and organized .
- Labeling: Clearly label each circuit on a chart or directly on the board to indicate the area or appliance it serves, complying with BS 7671 or local standards .

#### Safety and Compliance

- Ensure the distribution box is type-tested and made of non-combustible material.
- Verify MCB and RCCB ratings match the load requirements.
- Conduct a safety inspection after wiring to check for short circuits, overloads, and proper earthing .
- Follow local electrical codes such as IEC 61439, BS 7671, or NEC depending on your region .

#### Best Practices

- Leave spare ways for future expansion.
- Maintain uniform spacing and proper tie-down of wires.
- Install SPD if sensitive equipment is connected or if required by risk assessment.
- Use RCBOs for circuits requiring individual RCD protection to prevent nuisance tripping . By following this sequence and adhering to safety standards, an 18-circuit distribution box can be wired efficiently, safely, and in compliance with regulatory requirements.

## Article Content

How to wire a DB – Distribution Board Wiring – Mechatrofice

The cable or wire size, the rating of breakers, fuse, etc depends on the type of wiring, purpose, and rating of loads. It

Circuit Breaker Wiring Configurations in Distribution Boxes

Learn circuit breaker wiring configurations for distribution boxes: 1P and 3P layouts, RCD/RCBO neutral paths, phase balance, cable

DIY Wiring a Consumer Unit and Installation

A Sub Circuit can be an electric cable distributing power to few lights, or a socket outlet/s through a MCB device or a Fuse in the

How to Install a Distribution Box—A Comprehensive Instruction

Distribution boxes are used for power distribution, circuit protection and cable management, while junction boxes are

## Contact Us

Continue your research online:

Website: <https://thegalleryselfcatering.co.za>

Technical inquiry: <https://thegalleryselfcatering.co.za/contact.html>

This document is for preliminary research. Verify specifications against current standards, product documentation and project requirements.

